

Electrical Power Engineering (2)

Code: EP2207

Lecture: 4

Tutorial: 4

Total: 8

Dr. Ahmed Mohamed Azmy

Department of Electrical Power and Machine Engineering
Tanta University - Egypt



Faculty of
Engineering



Tanta University

Per Unit quantities

Steps of converting actual single-phase system to the per unit quantities:

- Choose MVA base $\mathbf{MVA_{base}}$ for the whole system
- Choose a kilo voltage base $\mathbf{kV_{base}}$ for one section
- Calculate the voltage base in other sections in the network using the transformation ratio of transformers
- Calculate the impedance base and current base using $\mathbf{MVA_{base}}$ and $\mathbf{kV_{base}}$ in each section

$$Z_{base} = \frac{V_{base}}{I_{base}} = \frac{V_{base}^2}{S_{base}}$$

$$I_{base} = \frac{S_{base}}{V_{base}}$$

Per Unit quantities

Steps of converting actual single-phase system to the per unit quantities:

- Calculate the pu value using the general equation

$$\text{Per unit value} = \frac{\text{actual value}}{\text{base value}}$$

Per-Unit Scaling for Three-Phase Systems

To convert the actual three-phase system to the per unit quantities, perform the following steps:

- **Choose** an apparent power base " $VA_{3\text{-base}}$ " for the three phase for all parts in the system
- **Choose** a line-to-line voltage base $V_{L\text{-base}}$ for one section in the circuit
- **Calculate** the voltage base in other sections in the network using the transformation ratio of transformers considering the method of winding connection

Per-Unit Scaling for Three-Phase Systems

To convert the actual three-phase system to the per unit quantities, perform the following steps:

- Calculate the impedance base and current base in terms of VA_{base} and V_{base} in each section of the power system using the following equations:

$$I_{base} = \frac{S_{3-base}}{\sqrt{3}V_{L-base}}$$

Per-Unit Scaling for Three-Phase Systems

To convert the actual three-phase system to the per unit quantities, perform the following steps:

For star connection:

$$Z_{\text{base}} = \frac{(V_{L-\text{base}})^2}{S_{3-\text{base}}}$$

For delta connection:

$$Z_{\text{base}} = 3 \frac{(V_{L-\text{base}})^2}{S_{3-\text{base}}}$$

- Calculate the pu value using the general equation

$$\text{Per - unit value} = \frac{\text{actual value}}{\text{base value}}$$

Per Unit quantities

Changing the base

If the values of the parameters are given for certain bases and it is required to calculate the values for other bases, a certain relation can be used

This relation modifies the old value according to the ratio between new and old bases according to the following relation:

$$X_{pu(new)} = X_{pu(old)} \frac{VA_{b(new)}}{VA_{b(old)}} \left(\frac{V_{b(old)}}{V_{b(new)}} \right)^2$$

Per Unit quantities

Example:

For the network shown, the data are:

Tr_1 : 20 MVA, 11/110 kV, $x = j0.12$ p.u.


G_1 : 20 MVA, 11 kV, $x = j0.4$ p.u.

Tr_2 : 10 MVA, 6/110 kV, $x = j0.15$ p.u.

G_2 : 10 MVA, 6 kV, $x = j0.35$ p.u.

Tr_3 : 5 MVA, 3/110 kV, $x = j0.1$ p.u.

G_3 : 5 MVA, 3 kV, $x = j0.3$ p.u.

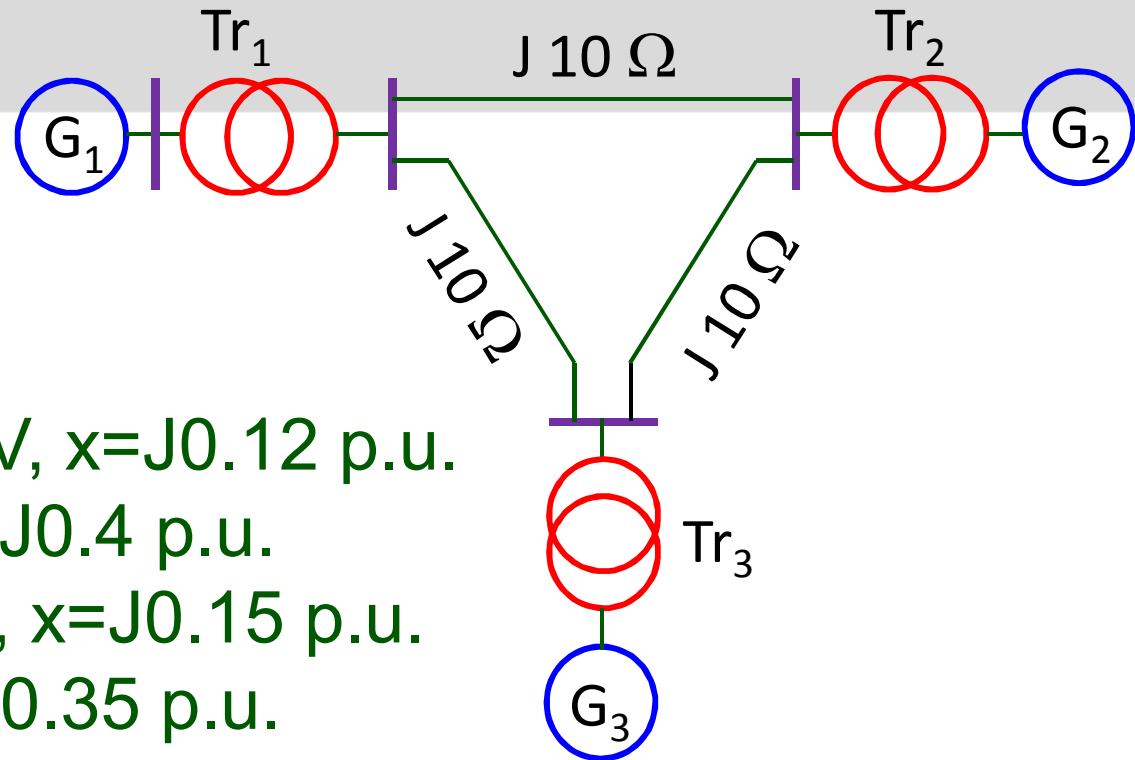

Draw the impedance diagram for the network assuming bases of 20 MVA and 11 kV in the G_1 area.

Per Unit quantities

Solution

$$\text{MVA}_b = 20 \text{ MVA}$$

$$\text{kV}_{b-I} = 11 \text{ kV}$$

$$\text{kV}_{b-II} = 110 \text{ kV}$$


$$\text{kV}_{b-III} = 6 \text{ kV}$$

$$\text{kV}_{b-IV} = 3 \text{ kV}$$

$$X_L = 10 * 20 / (110)^2 = j 0.017$$

$$X_{g1} = 0.4 * 20 / 20 (11/11)^2 = j 0.4$$
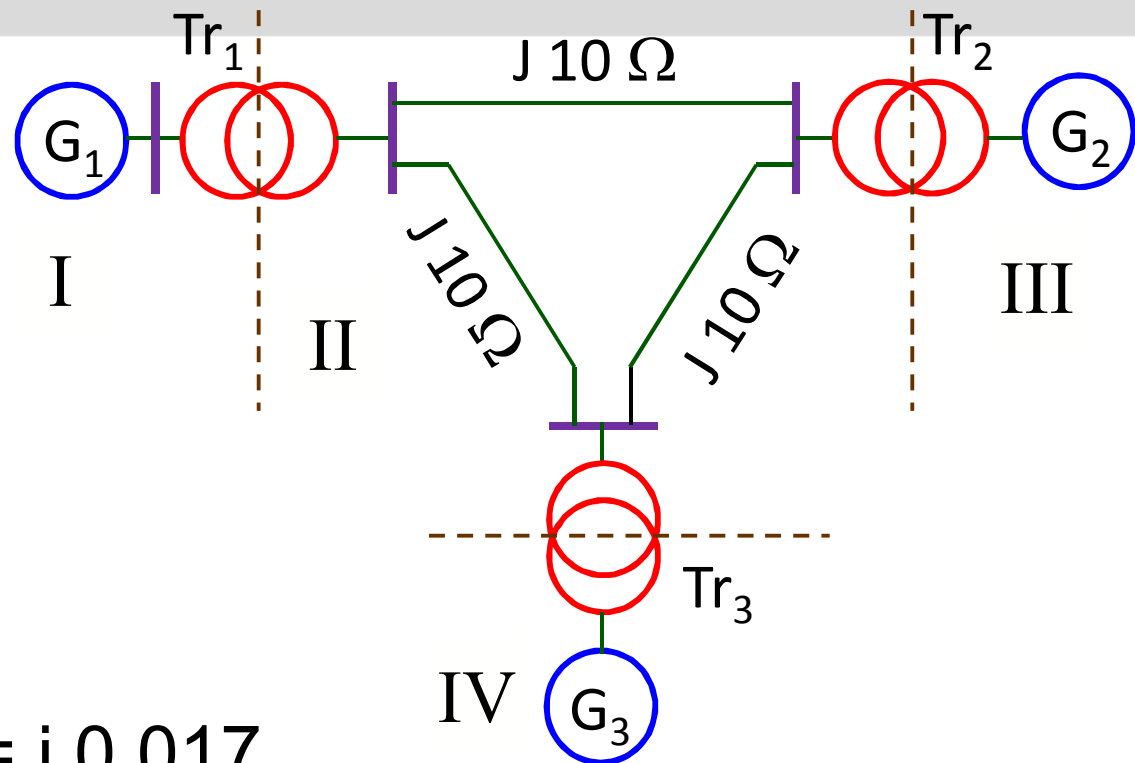
$$X_{g2} = 0.35 * 20 / 10 (6/6)^2 = j 0.7$$




Per Unit quantities

Solution

$$X_{g3} = 0.3 \frac{20}{5} \left(\frac{3}{3} \right)^2 = j1.2$$
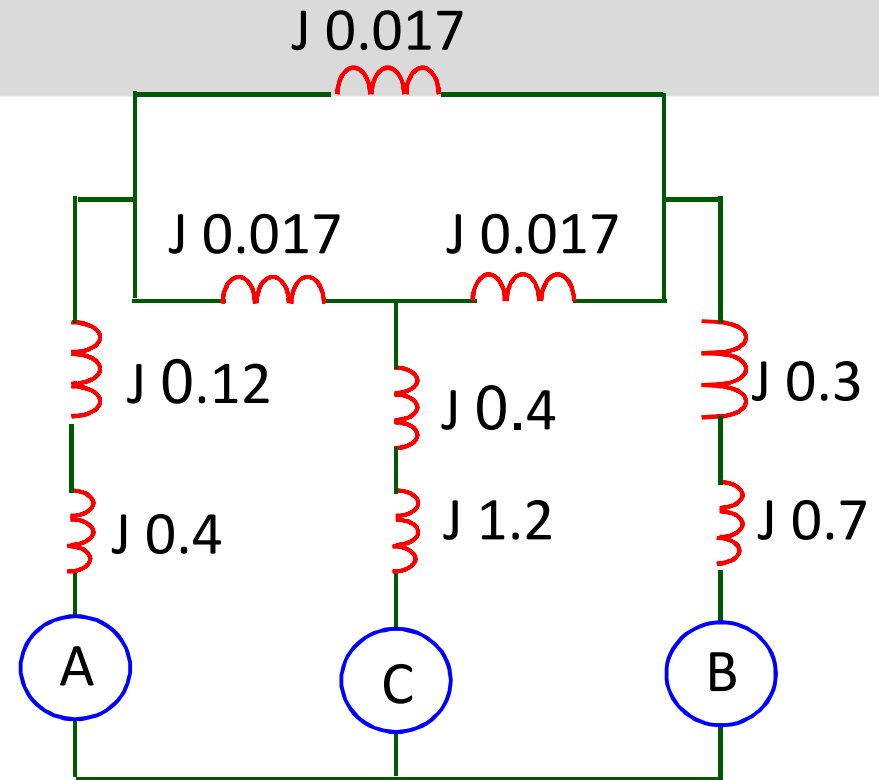
$$X_{tr1} = 0.12 \frac{20}{20} \left(\frac{110}{110} \right)^2 = j0.12$$




$$X_{tr2} = 0.15 * 20 / 10 (110/110)^2 = j 0.3$$

$$X_{tr3} = 0.1 * 20 / 5 (110/110)^2 = j 0.4$$

Example: The power system shown in the figure has the following ratings:

Generator G_1	200 MVA, 20 kV, $X_d = 15\%$
Generator G_2	300 MVA, 18 kV, $X_d = 20\%$
Generator G_3	300 MVA, 20 kV, $X_d = 20\%$
Transformer T_1	300 MVA, 220Y/22 kV, $X_d = 10\%$
Transformer T_2	Three single-phase units each rated 100 MVA, 130 Y / 25 Δ kV, $X = 10\%$
Transformer T_3	300 MVA, 220/22 kV, $X = 10\%$

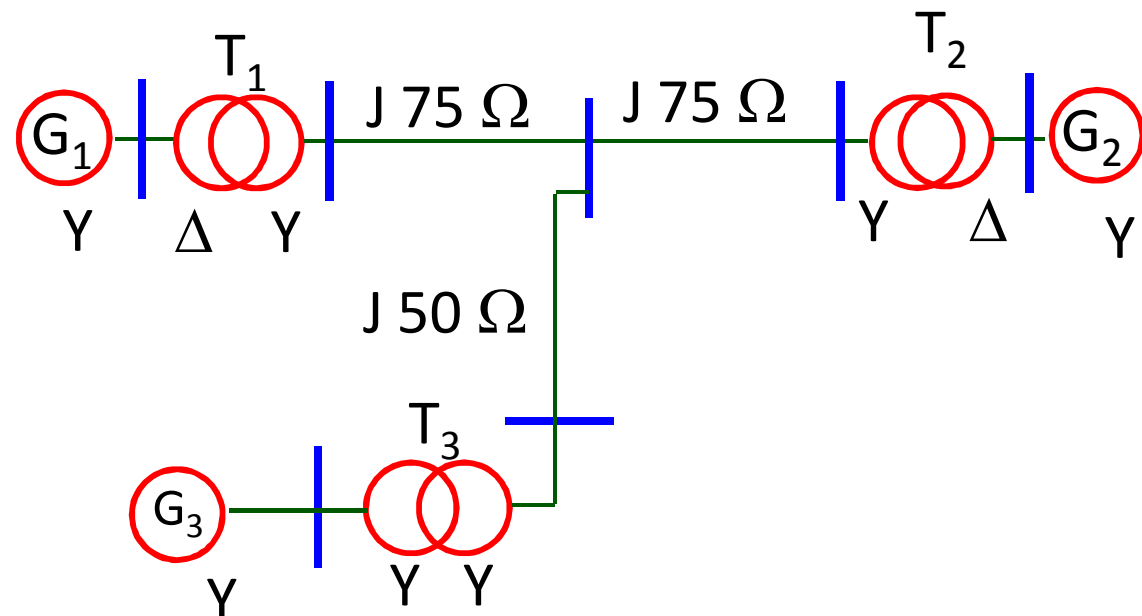The transmission line reactances are as indicated in the figure. Draw the reactance diagram in per unit choosing the generator 3 circuit as the base.



$MVA_{base} = 300 \text{ MVA}$


H.V.S. of transformer T_2 is Y connected

Its rated line to line voltage is $\sqrt{3} \times 130 = 225 \text{ kV}$

L.V.S. is connected in $\Delta \rightarrow$ Its line voltage is 25 kV

$V_{b, III} = 20 \text{ kV},$

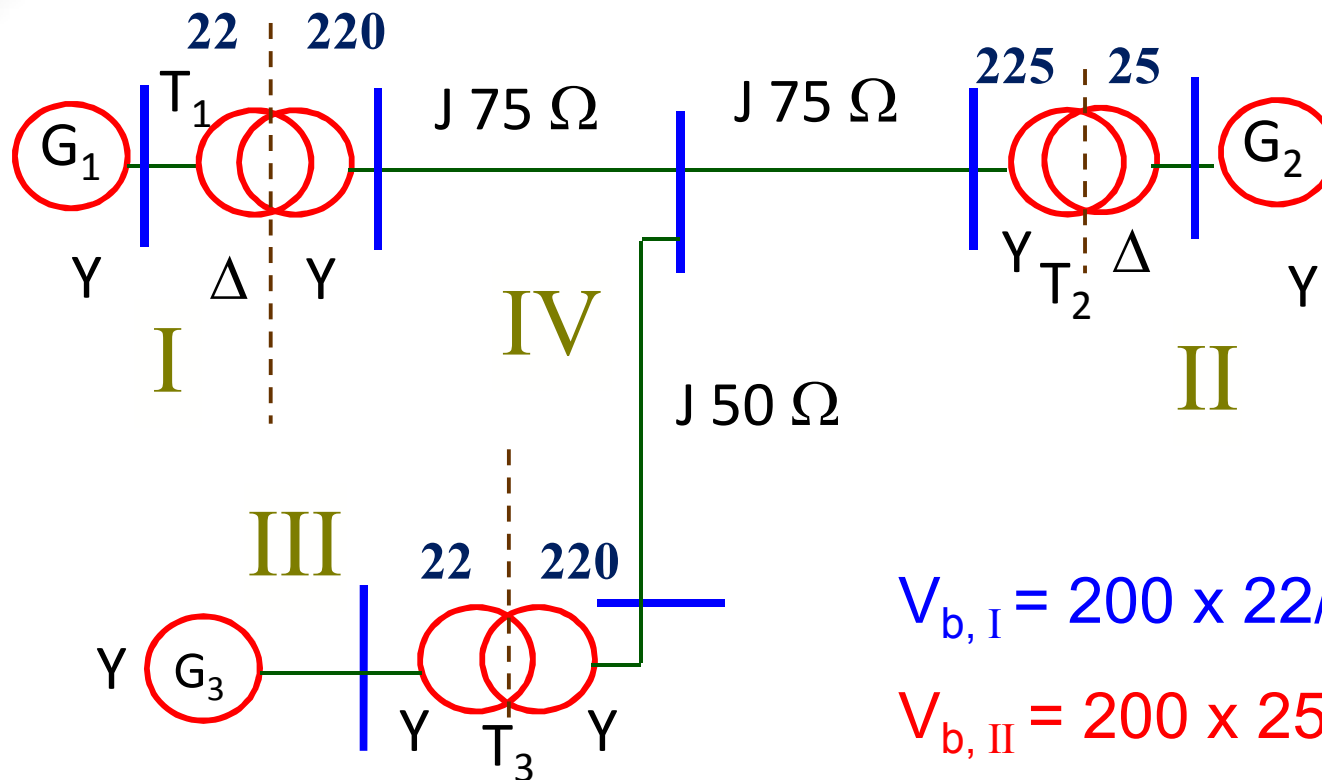$V_{b, IV} = 20 \times 220/22 = 200 \text{ kV}$



$$V_{b, I} = 200 \times 22/220 = 20 \text{ kV}$$

$$V_{b, II} = 200 \times 25/225 = 22.22 \text{ kV}$$

$$V_{b, I} = 200 \times 22/220 = 20 \text{ kV}$$

$$V_{b, II} = 200 \times 25/225 = 22.22 \text{ kV}$$

Generator G_1	$X_{G1} = 0.15 \times \frac{300}{200} = 0.225$
Generator G_2	$X_{G2} = 0.2 \times \left(\frac{18}{22.22} \right)^2 = 0.1312$
Generator G_3	$X_{G3} = 0.2$
Transformer T_1	$X_{T1} = 0.1 \times \left(\frac{220}{200} \right)^2 = 0.121$

Transformer T ₂	$X_{T2} = 0.1 \times \left(\frac{25}{22.22} \right)^2 = 0.1266$
----------------------------	--

Transformer T ₃	$X_{T3} = 0.1 \times \left(\frac{22}{20} \right)^2 = 0.121$
----------------------------	--

$$Z_{base} = \frac{(200 \times 10^3)^2}{300 \times 10^6} = 133.33$$

$$X_{j75} = \frac{75}{133.33} = 0.5625$$

$$X_{j50} = \frac{50}{133.33} = 0.375$$

